

CMPE 460 Laboratory Exercise 6

Motor Control

Mohammed Fareed
Trent Wesley
Performed: October 18, 2023
Submitted: November 1, 2023

Lab Section: 1
Instructor: Prof. Hussin Ketout
TA: Andrew Tevebaugh
Colin Vo

Lecture Section: 1
Professor: Prof. Hussin Ketout

By submitting this report, you attest that you neither have given nor have received any assistance (including writing, collecting data, plotting figures, tables or graphs, or using previous student reports as a reference), and you further acknowledge that giving or receiving such assistance will result in a failing grade for this course.

Your Signature: _____

Lab Description

This laboratory exercise involved interfacing the MSP432 with a DC motor, a stepper motor, and a servo. First, the Timer A module was used to generate a PWM signal. Specifically, a 20% duty cycle signal with a frequency of 10kHz was generated and viewed with an oscilloscope. Next, a DC motor was controlled. A SN754410 H-bridge IC was utilized to control the 10V power supply voltage with the 3.3V control voltage from the MSP432. The stepper motor was operated in full step, low torque mode by the MSP432 with a ULN2068B Darlington array IC. It was controlled by periodically switching which coils turned on based on the phase. The last type of motor tested was the servo motor. This was controlled by providing a 50Hz PWM signal with a pulse width between 1ms and 2ms. Finally, knowledge gained from testing these motors was used to simultaneously control two DC motors and a servo.

Wiring Diagrams

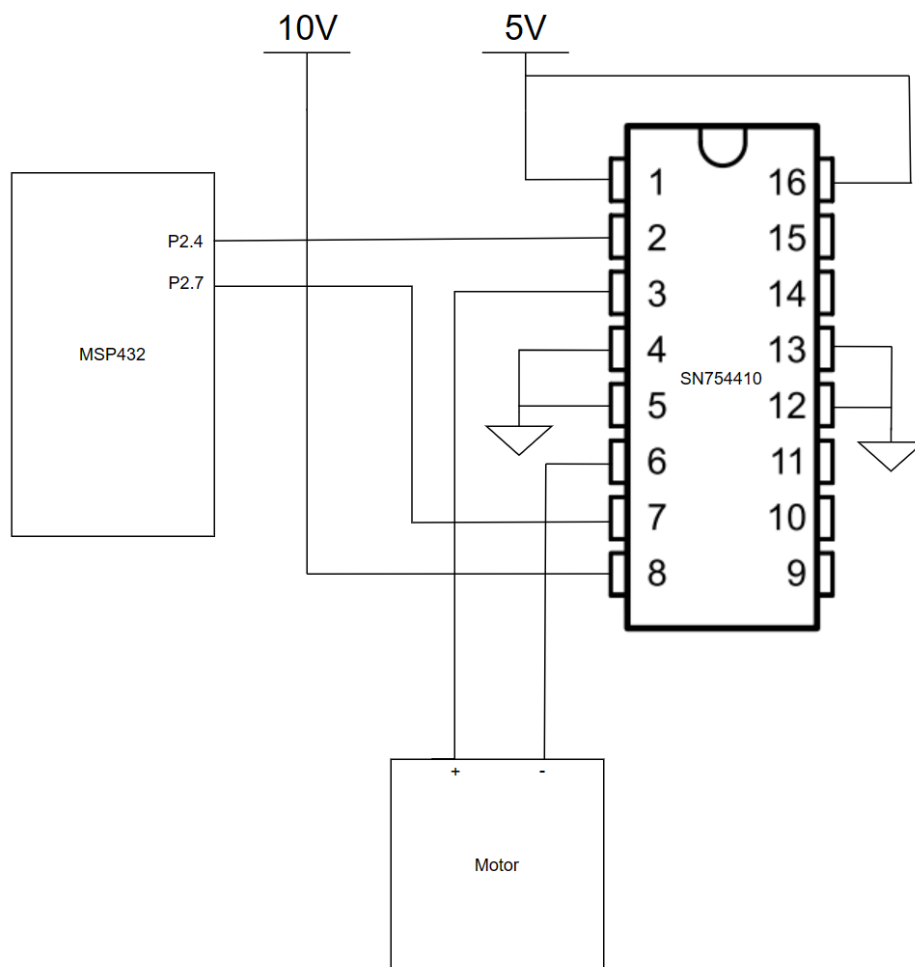


Figure 1: DC Motor Wiring

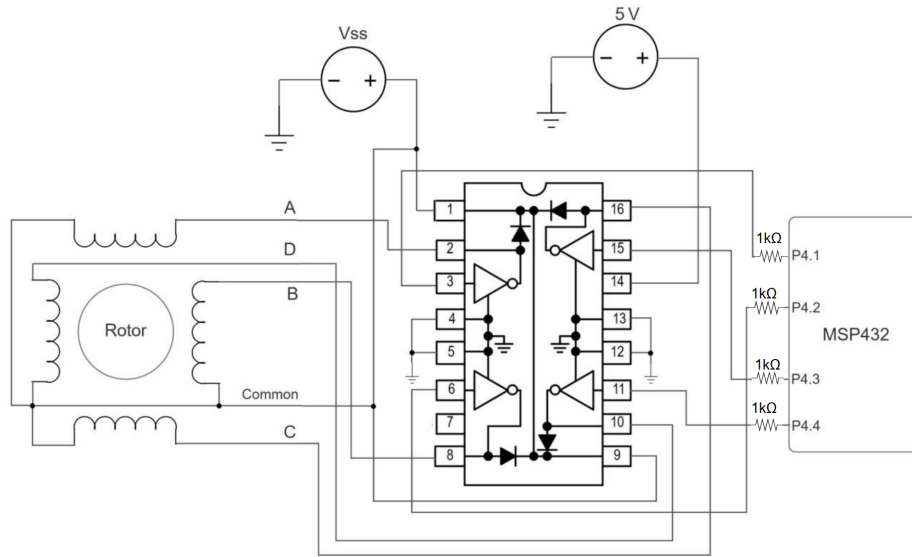


Figure 2: Stepper Motor Wiring

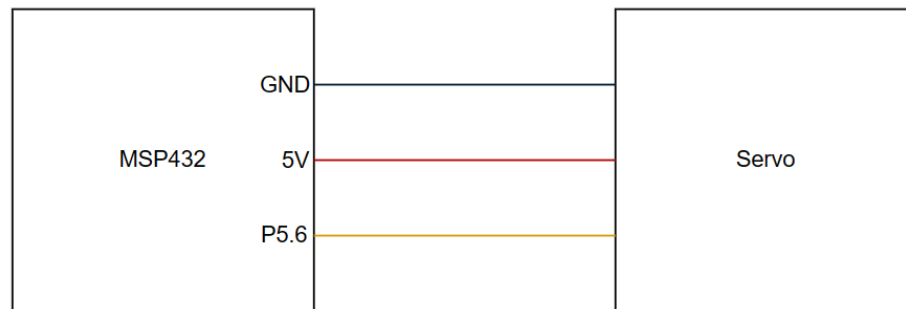


Figure 3: Servo Wiring

Prelab Questions

Part 1:

Motor stall torque in oz-in and in kg-cm before reduction

$$4.5 \text{ kgcm} / 30 = 0.15 \text{ kgcm} = 2.08 \text{ oz-in}$$

Maximum current draw

$$1.4 \text{ A}$$

Maximum motor turn speed before reduction

$$0.2 \text{ kRPM} * 30 = 6 \text{ kRPM}$$

Maximum torque in oz-in after gear reduction

4.5 kgcm = 66.66 oz-in

Maximum turn speed in kRPM after gear reduction
0.2 kRPM

Part 2:

What is the purpose of the diodes in this circuit?

When the motor turns off or changes direction, it can generate a voltage spike due to its inductive nature. These diodes provide a safe path for the induced current to flow, preventing damage to the transistors or other components in the circuit.

What is the purpose of the capacitor in this circuit?

The transistor serves decoupling purposes. It can absorb voltage spikes and noise produced by the motor, ensuring that this noise doesn't propagate back into the rest of the circuit or power supply.

Why are the transistors in each side of the circuit in pairs?

The pairs form a Darlington pair. This results in a very high current gain, allowing a small input current (from the microcontroller) to control a much larger output current, which can drive the motor.

Why use 2N3904/2N3906 for some transistors and TIP31/TIP42 for others?

The 2N3904/2N3906 are general purpose and can only handle low current. The TIP31/TIP42 are power transistors that can handle the high current needed to drive the motor.

Oscilloscope Captures

Figure 4 shows the PWM output waveform measured with an oscilloscope.

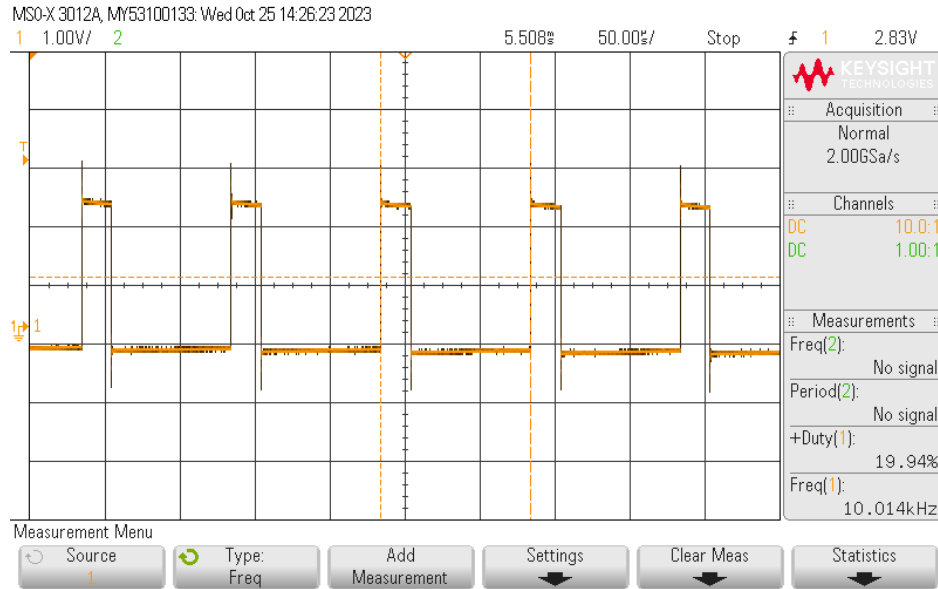


Figure 4: PWM Waveform

As shown in this diagram, the MSP432 PWM port outputted a 10kHz signal with a 20% duty cycle as intended. PWM was used to control the input to a DC motor. The input and output to and from the H-bridge is shown in Figure 5.

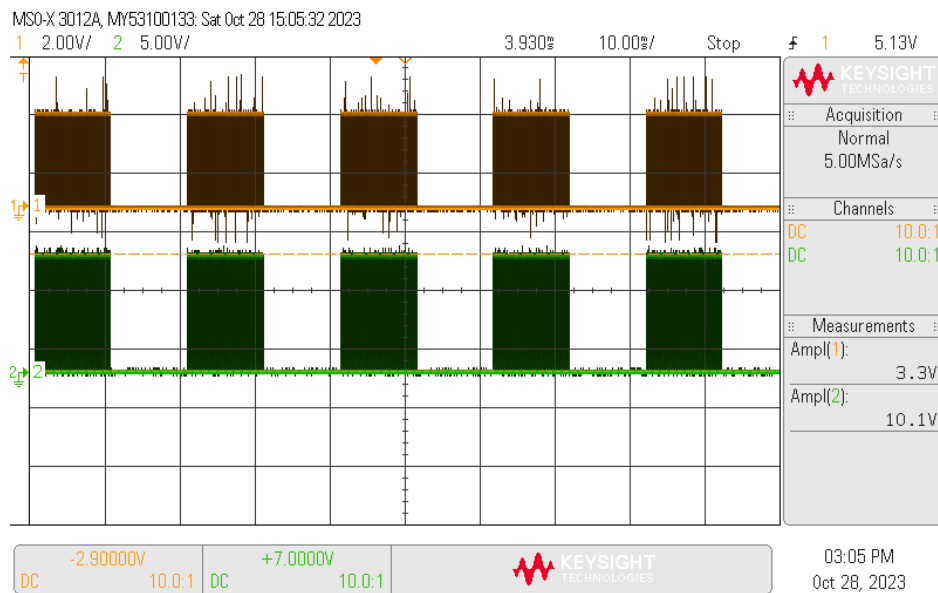


Figure 5: Motor Input Output Waveform

Figure 5 shows the 10V output from the H-bridge to the motor corresponds with the 3.3V input to the H-bridge, suggesting that the circuit is functioning as expected. Figure 6 shows the PWM input for the control signal to the servo.

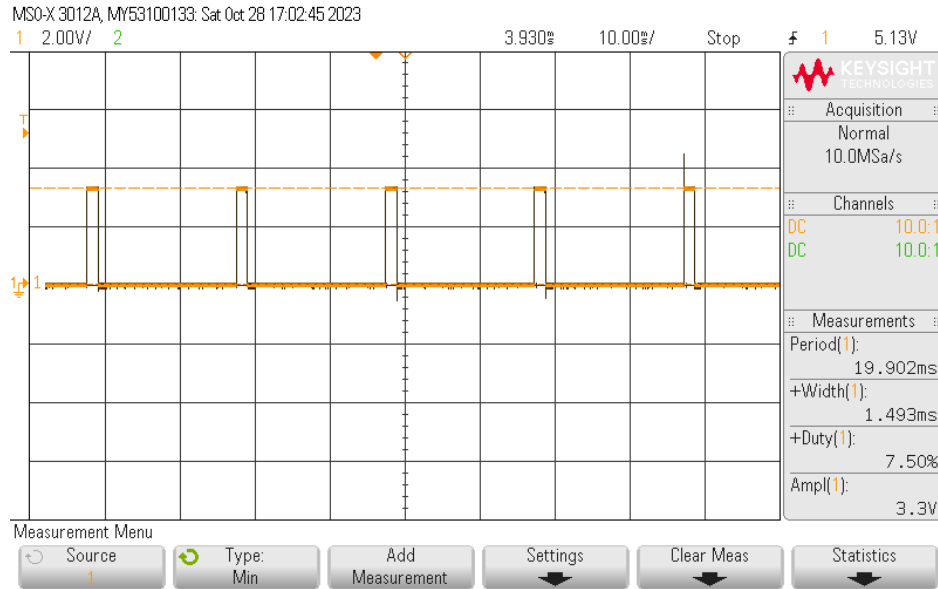


Figure 6: Servo Input Waveform

The servo input shown has a period of 20ms and a pulse width of 1.5ms. This input moves the servo to the center position.

Code Explanation

Code was written to control a DC motor, a stepper motor, and a servo motor. For the DC motor, the MSP432 was initialized to generate two PWM signals with a 10kHz frequency and a 20% duty cycle using Timer A0. The code then entered an infinite loop where the duty cycle of the PWM signals was changed to control the speed of the motor. The direction of the motor was changed by switching the PWM and 0V signals to the H-bridge.

For the stepper motor, the MSP432 was initialized to output the control signals for the motor's coils using port 4. The code then entered an infinite loop where the coils were turned on and off in a specific order to control the direction of the motor.

For the servo motor, the MSP432 was initialized to generate a PWM signal with a 50Hz frequency and a duty cycle between 5% and 10%. The code then entered an infinite loop where the pulse width of the PWM signal was changed to control the position of the servo. The DC motors and servo motor code was combined and modified to work with the provided car. The MSP432 was initialized to generate 5 PWM to control 2 DC motors at 10kHz using Timer A0 and one servo motor for steering using Timer A2. The code then entered an infinite loop where the duty cycle of the A0 PWM signals was changed to control the speed of the motors and the A2 pulse width of the PWM signal was changed to control the position of the servo.

Questions

Explain how to change speed and direction of turn of the DC motor.

To change the speed of the DC motor, the duty cycle of the PWM signal from the MSP432 to the H-bridge can be changed. To reverse the direction of the DC motor, the PWM and 0V signals to the H-bridge can be switched.

Describe an alternate method that uses only one PWM line and one GPIO line.

An H-bridge can be used to control the direction of the motor. The PWM signal can be used to control the speed of the motor. The GPIO can be used to control the H-bridge to switch which terminal is grounded and which is connected to the PWM line. This allows the GPIO to control the direction, allowing a single PWM to control the speed for both directions.

Which stepping mode does the code use?

Full step mode was used.

Exercise 6: Motor Control

Student's Name: Mohammed Faried Trent Wesley Section: 1

PreLab		Point Value	Points Earned	Comments
PreLab	Motor Calculations	10	10	AST 10/17
	H-Bridge Questions	10	10	AST 10/17

Demo		Point Value	Points Earned	Date
Demo	20% Duty Cycle at 10kHz	10	10	AST 10/25
	DC Motor Functionality	5	5	MT 10/30
	Stepper Motor Functionality	5	5	MT
	Servo Motor Functionality	5	5	MT 10/30
	Simultaneous TI Car Motors-Servo Motor	15		

To receive any grading credit students must earn points for both the demonstration and the report.